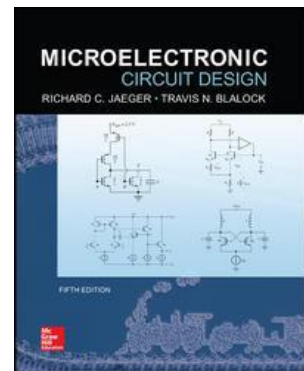

Chapter 0

Introduction to Electronics

Microelectronic Circuit Design

Richard C. Jaeger
Travis N. Blalock

(c) 2015 McGraw-Hill Education.
All rights reserved



BT 1


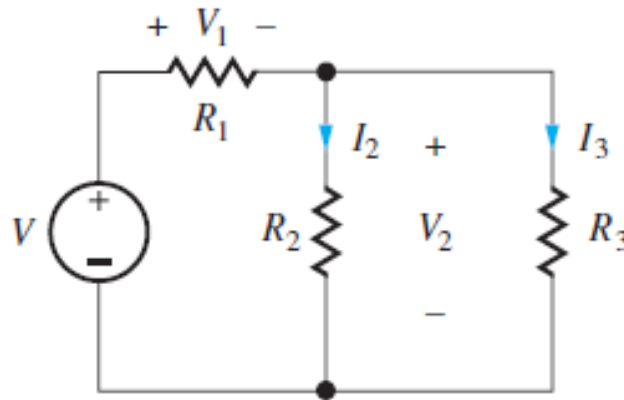


Figure P1.22

Use voltage and current division to find V_1 , V_2 , I_2 , and I_3 in the circuit in Fig. P1.22 if $V = 8 \text{ V}$, $R_1 = 30 \text{ k}\Omega$, $R_2 = 24 \text{ k}\Omega$, and $R_3 = 15 \text{ k}\Omega$

BT 1 (Sol.)

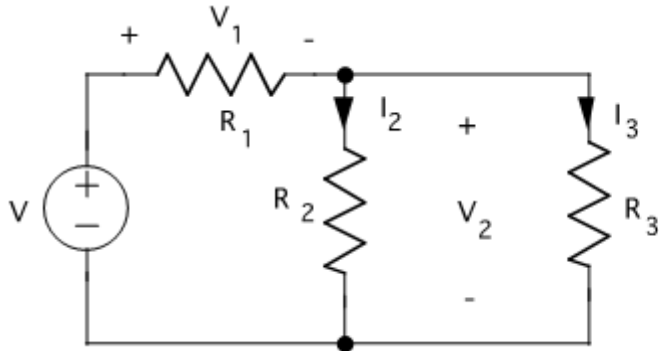

$V = 8\text{ V}$, $R_1 = 30\text{ k}\Omega$, $R_2 = 24\text{ k}\Omega$ and $R_3 = 15\text{ k}\Omega$.

$$V_1 = 8V \frac{30k\Omega}{30k\Omega + (24k\Omega \parallel 15k\Omega)} = 8V \frac{30k\Omega}{30k\Omega + 9.23k\Omega} = 6.12\text{ V}$$

$$V_2 = 8V \frac{24k\Omega \parallel 15k\Omega}{30k\Omega + (24k\Omega \parallel 15k\Omega)} = 1.88\text{ V} \quad \text{Checking: } 6.12 + 1.88 = 8.00\text{ V}$$

$$I_2 = I_1 \frac{R_3}{R_2 + R_3} = \left(\frac{8V}{30k\Omega + 9.23k\Omega} \right) \frac{15k\Omega}{24k\Omega + 15k\Omega} = 78.4\text{ mA}$$

$$I_3 = I_1 \frac{R_2}{R_2 + R_3} = \left(\frac{8V}{30k\Omega + 9.23k\Omega} \right) \frac{24k\Omega}{24k\Omega + 15k\Omega} = 125\text{ mA}$$

$$\text{Checking: } I_1 = \frac{8V}{30k\Omega + 9.23k\Omega} = 204\text{ mA} \quad \text{and} \quad I_1 = I_2 + I_3$$

BT 2

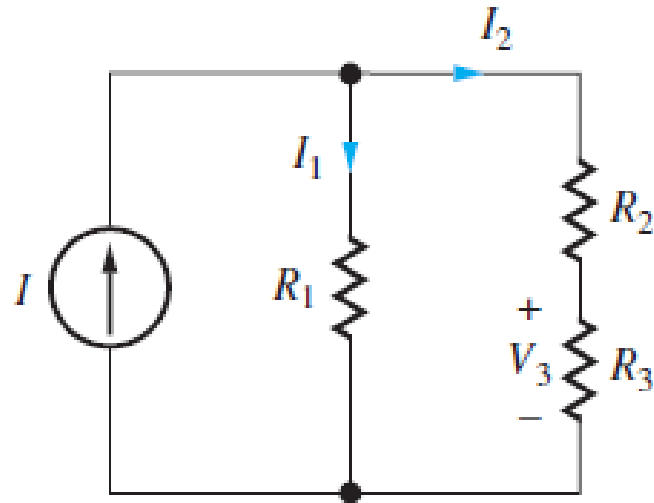


Figure P1.24

Use current and voltage division to find I_1 , I_2 , and V_3 in the circuit in Fig. P1.24 if $I = 200 \mu\text{A}$, $R_1 = 150 \text{ k}\Omega$, $R_2 = 68 \text{ k}\Omega$, and $R_3 = 82 \text{ k}\Omega$.

BT 2 (Sol.)

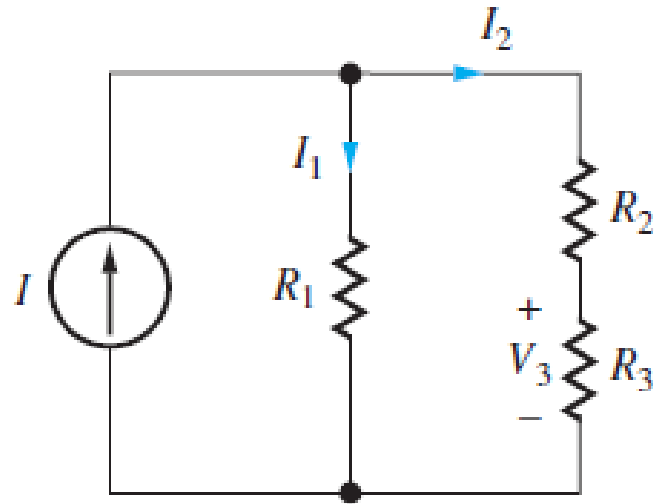



Figure P1.24

$$I_2 = 200\text{mA} \left(\frac{150\text{k}\Omega}{150\text{k}\Omega + 150\text{k}\Omega} \right) = 100\text{mA} \quad I_3 = 200\text{mA} \left(\frac{150\text{k}\Omega}{150\text{k}\Omega + 150\text{k}\Omega} \right) = 100\text{mA}$$


$$V_3 = 200\text{mA} (150\text{k}\Omega \parallel 150\text{k}\Omega) \left(\frac{82\text{k}\Omega}{68\text{k}\Omega + 82\text{k}\Omega} \right) = 8.2\text{V}$$

$$\text{Checking: } I_1 + I_2 = 200\text{mA} \quad \text{and} \quad I_2 R_2 = 100\text{mA} (82\text{k}\Omega) = 8.2\text{V}$$

BT 3

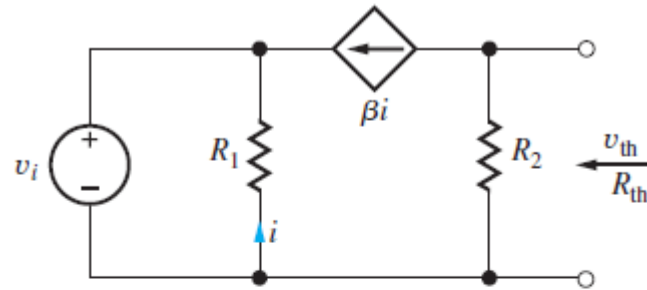

(a)

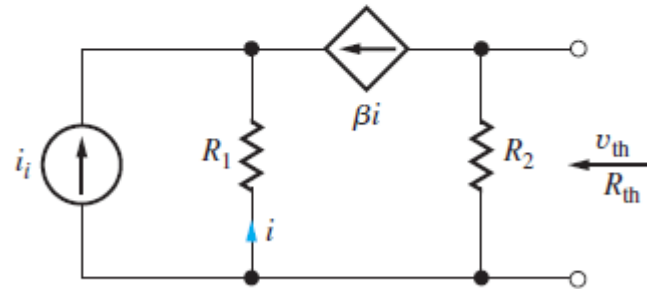


(b)


Figure P1.27

- a) Find the Norton equivalent representation of the circuit in Fig. P1.27(a, b) if $\beta = 150$, $R_1 = 39 \text{ k}\Omega$, and $R_2 = 100 \text{ k}\Omega$.
- b) Find the Thevenin equivalent representation of the circuit in Fig. P1.27(a,b) if $\beta = 120$, $R_1 = 56 \text{ k}\Omega$, and $R_2 = 75 \text{ k}\Omega$.

BT 3 (Sol. Norton a)

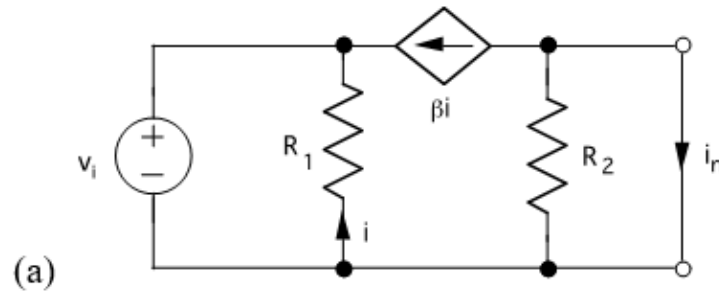

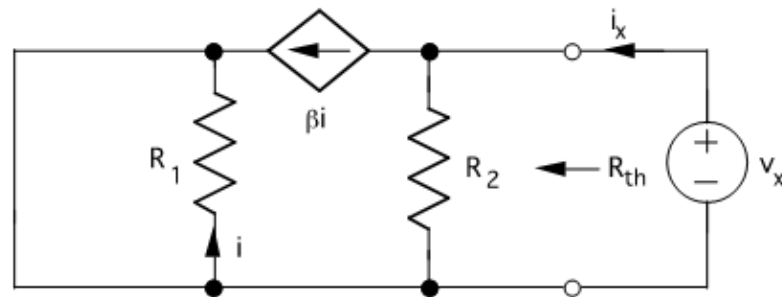
$$i_n = -\beta i \quad \text{but} \quad i = -\frac{v_i}{R_1} \quad \text{and} \quad i_n = \frac{\beta}{R_1} v_i = \frac{150}{39 \text{ k}\Omega} v_i = 3.85 \times 10^{-3} v_i$$




$$R_{th} = \frac{v_x}{i_x} ; \quad i_x = \frac{v_x}{R_2} + \beta i \quad \text{but} \quad i = 0 \quad \text{since} \quad v_{R_1} = 0. \quad R_{th} = R_2 = 100 \text{ k}\Omega$$

$$3.85 \times 10^{-3}$$

Norton equivalent circuit:

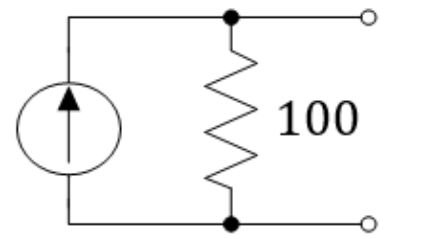


BT 3 (Sol. Norton b)

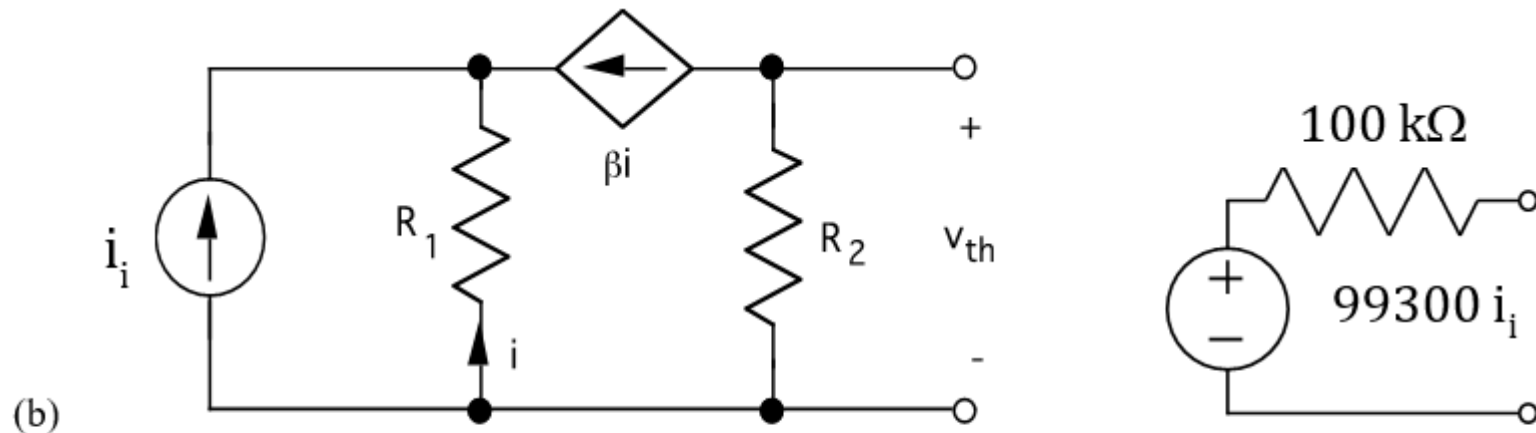


$$v_{th} = v_{oc} = -\beta i R_2 \quad \text{where} \quad i + \beta i + i_i = 0 \quad \text{and} \quad v_{th} = R_2 \left(\frac{\beta}{\beta + 1} \right) i_i = 100 \text{ k}\Omega \left(\frac{150}{151} \right) i_i = 99300 i_i$$

R_{th} is found in part (a).


BT 3 (Sol. Thevenin a)

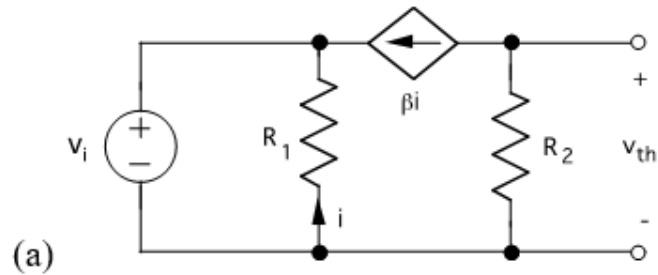
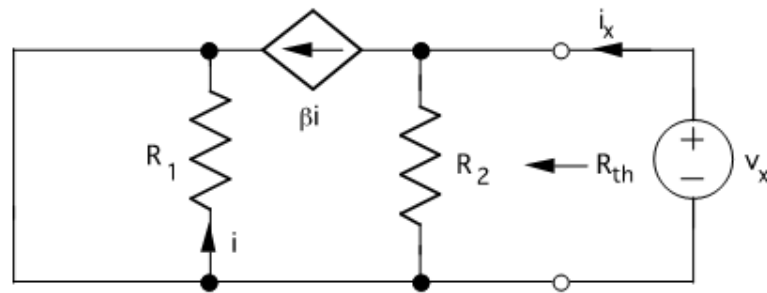
$$v_{th} = v_{oc} = -\beta i R_2 \quad \text{but} \quad i = -\frac{v_i}{R_1} \quad \text{and} \quad v_{th} = \beta v_i \frac{R_2}{R_1} = 120 v_i \frac{56k\Omega}{75k\Omega} = 89.6 v_i$$



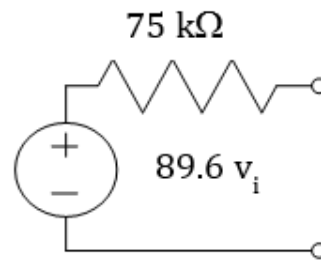
$$R_{th} = \frac{v_x}{i_x} ; \quad i_x = \frac{v_x}{R_2} + \beta i \quad \text{but} \quad i = 0 \quad \text{since} \quad v_{R_1} = 0. \quad R_{th} = R_2 = 75 \text{ k}\Omega$$




Thévenin equivalent circuit:


BT 3 (Sol. Thevenin b)

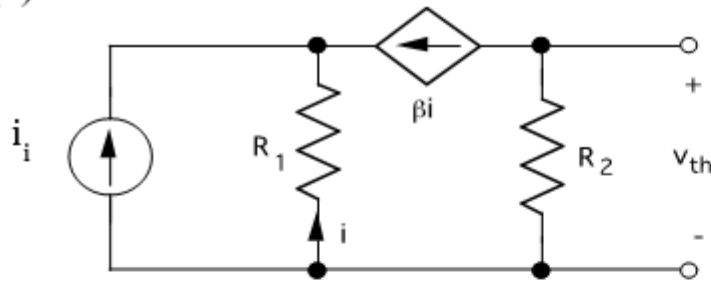
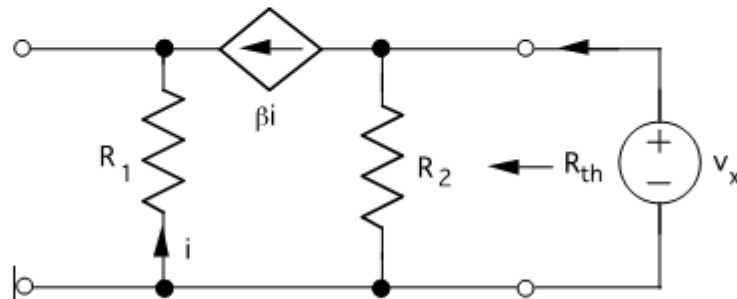
$$v_{th} = v_{oc} = -\beta i R_2 \quad \text{where} \quad i + \beta i + i_i = 0 \quad \text{and} \quad v_{th} = R_2 \left(\frac{\beta}{\beta+1} \right) i_i = 75 \text{ k}\Omega \left(\frac{120}{121} \right) i_i = 74400 i_i$$



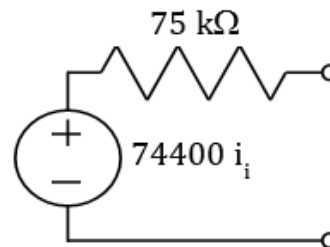
$$R_{th} = \frac{v_x}{i_x} ; \quad i_x = \frac{v_x}{R_2} + \beta i \quad \text{but} \quad i + \beta i = 0 \quad \text{so} \quad i = 0 \quad \text{and} \quad R_{th} = R_2 = 75 \text{ k}\Omega$$




Thévenin equivalent circuit:

BT 4

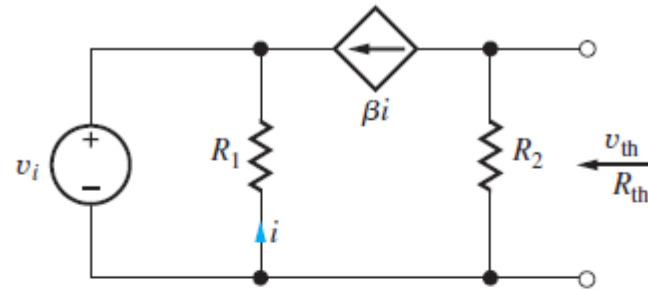

(a)


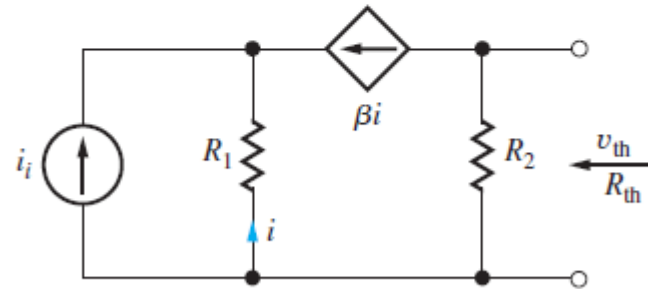


(b)

Figure P1.27

What is the resistance presented to source v_i by the circuit in Fig. P1.27(a,b) if $\beta = 75$, $R_1 = 100 \text{ k}\Omega$, and $R_2 = 39 \text{ k}\Omega$?

BT 4 (Sol.)

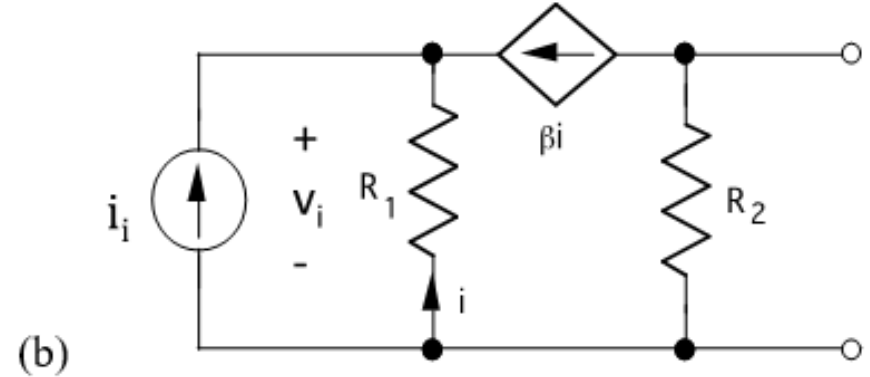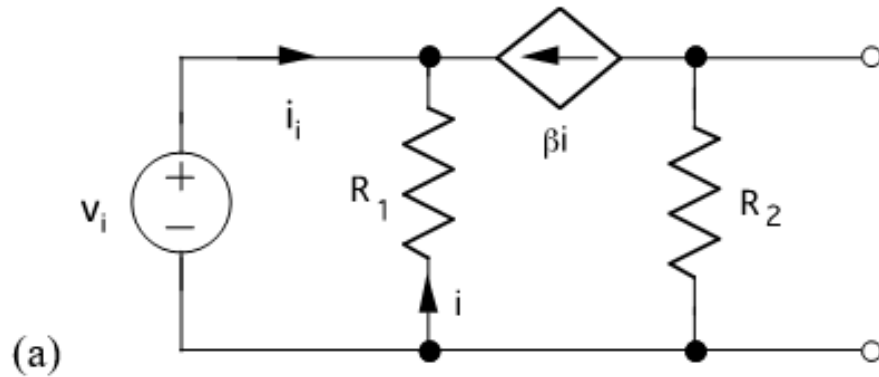

$$(a) \quad i_i = \frac{v_i}{R_1} - \beta i = \frac{v_i}{R_1} + \beta \frac{v_i}{R_1} = v_i \frac{\beta + 1}{R_1} \quad R = \frac{v_i}{i_i} = \frac{R_1}{\beta + 1} = \frac{100k\Omega}{76} = 1.32 \text{ k}\Omega$$

(b) Source is i_i in part (b).

$$v_i = -iR_1 \quad \text{and} \quad i_i = -i - \beta i = -(\beta + 1)i \quad R = \frac{v_i}{i_i} = -\frac{-1}{\beta + 1} R_1 = \frac{100k\Omega}{76} = 1.32 \text{ k}\Omega$$

BT 5

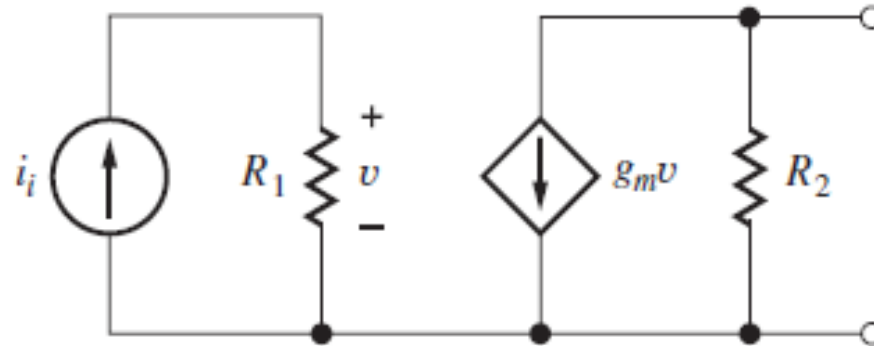


Figure P1.30

Find the Th'evenin equivalent representation of the circuit in Fig. P1.30 if $g_m = .0025 \text{ S}$, $R_1 = 200 \text{ k}\Omega$, and $R_2 = 2 \text{ M}\Omega$

BT 5 (Sol.)

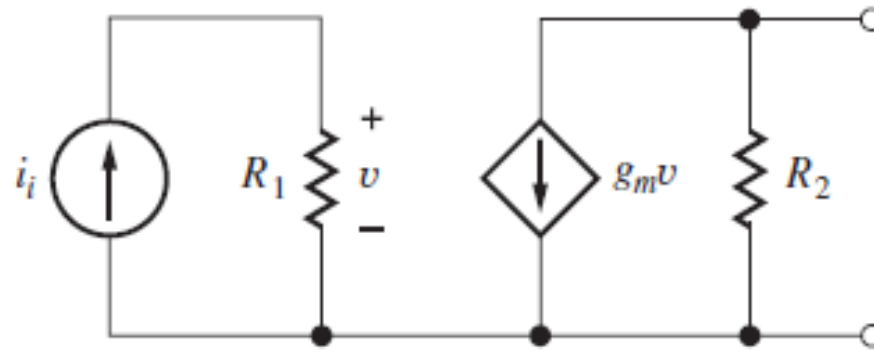


Figure P1.30

The open circuit voltage is $v_{th} = -g_m v R_2$ where $v = +i_i R_1$.

$$v_{th} = -g_m R_1 R_2 i_i = -(0.0025)(2 \times 10^5)(2 \times 10^6) i_i = 1.0 \times 10^9 i_i$$

For $i_i = 0$, $v = 0$, and $R_{th} = R_2 = 2 \text{ MW}$

BT 6

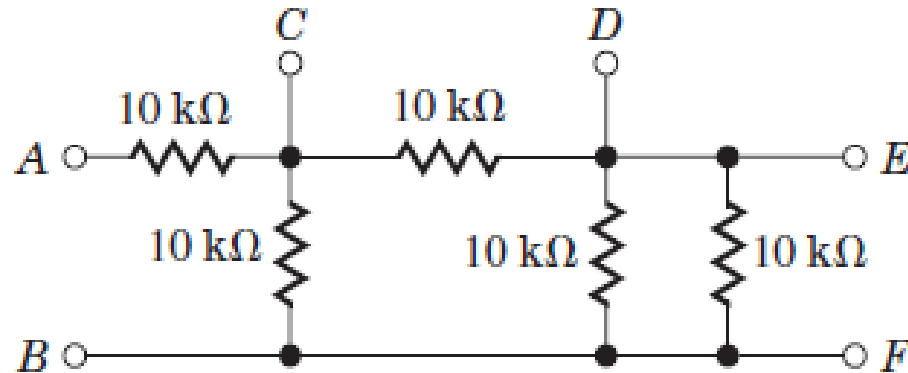


Figure P1.31

- (a) What is the equivalent resistance between terminals A and B in Fig. P1.31?
- (b) What is the equivalent resistance between terminals C and D ?
- (c) What is the equivalent resistance between terminals E and F ?
- (d) What is the equivalent resistance between terminals B and D ?

BT 6 (Sol.)

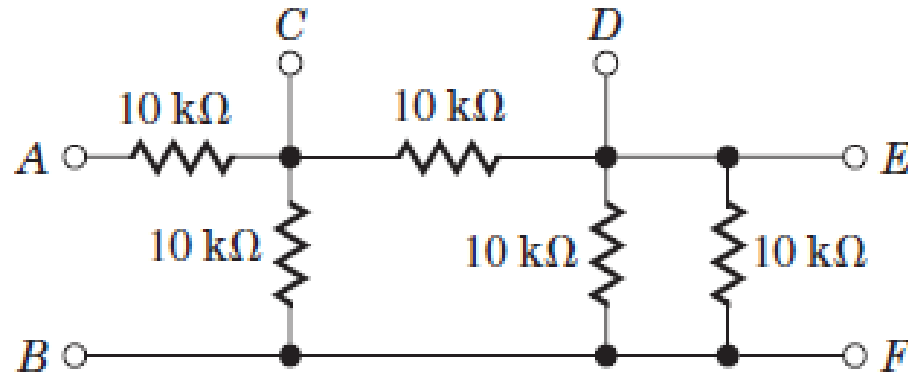


Figure P1.31

$$(a) R_{AB} = 10k\Omega + 10k\Omega \parallel \left[10k\Omega + (10k\Omega \parallel 10k\Omega) \right] = 16 k\Omega$$

$$(b) R_{CD} = 10k\Omega \parallel \left[10k\Omega + (10k\Omega \parallel 10k\Omega) \right] = 6 k\Omega$$

$$(c) R_{EF} = 10k\Omega \parallel 10k\Omega \parallel (10k\Omega + 10k\Omega) = 4 k\Omega$$

$$(d) \text{ Terminals B \& D are the same as E \& F. } R_{BD} = 4 k\Omega$$

BT 7

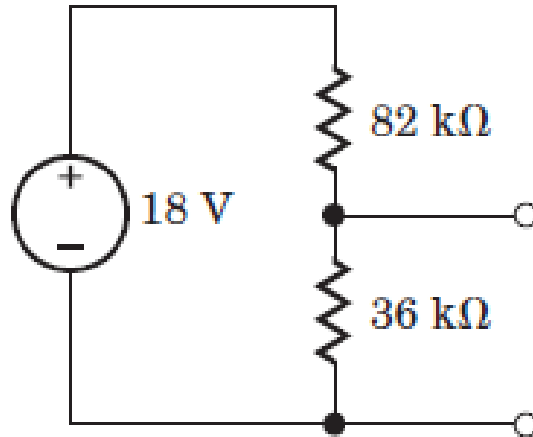


Figure P1.32

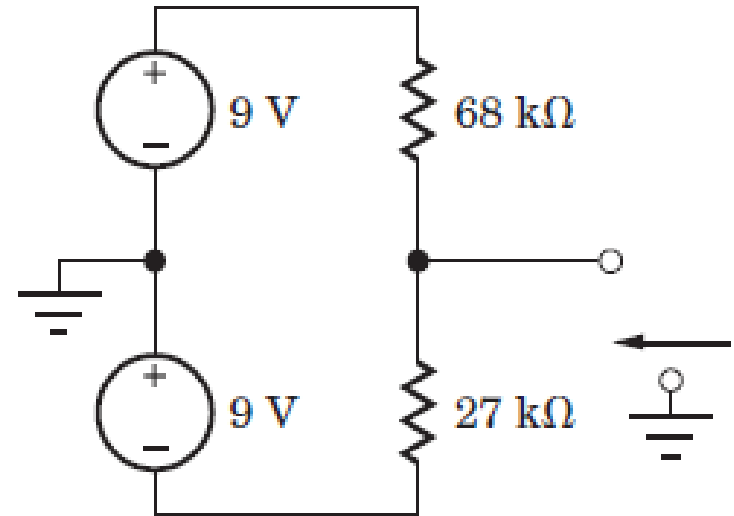


Figure P1.33

- (a) Find the Thévenin equivalent circuit for the network in Fig. P1.32, 33.
- (b) What is the Norton equivalent circuit?

BT 7 (Sol. Fig. 1.33)

(a) The open - circuit voltage is $v_{th} = 18V \frac{36k\Omega}{82k\Omega + 36k\Omega} = 5.49 \text{ V}$

The Thevenin equivalent resistance is $R_{th} = 36k\Omega \parallel 82k\Omega = 25.0 \text{ k}\Omega$

(b) The short - circuit current is $i_n = \frac{18V}{82k\Omega} = 220 \text{ }\mu\text{A}$

The Thevenin equivalent resistance is $R_{th} = 36k\Omega \parallel 82k\Omega = 25.0 \text{ k}\Omega$

Checking : $i_n R_{th} = 5.49 \text{ V}$ which equals v_{th} and is correct.

BT 7 (Sol. Fig. 1.32)

(a) The open - circuit voltage is $v_{th} = -9V + I \times 27k\Omega = -9V + \left(\frac{18V}{68k\Omega + 27k\Omega}\right)27k\Omega = -3.88 V$

The open - circuit voltage is also $v_{th} = +9V - I \times 68k\Omega = -9V + \left(\frac{18V}{68k\Omega + 27k\Omega}\right)68k\Omega = -3.88 V$

Using voltage division yields $v_{th} = -9V + 18V\left(\frac{27k\Omega}{68k\Omega + 27k\Omega}\right) = -3.88 V$

Using voltage division yields $v_{th} = +9V - 18V\left(\frac{68k\Omega}{68k\Omega + 27k\Omega}\right) = -3.88 V$

The Thevenin equivalent resistance is $R_{th} = 27k\Omega \parallel 68k\Omega = 19.3 k\Omega$

(b) The short - circuit current is $i_n = \frac{9V}{68k\Omega} - \frac{9V}{27k\Omega} = -201 \mu A$

The Thevenin equivalent resistance is $R_{th} = 27k\Omega \parallel 68k\Omega = 19.3 k\Omega$

Checking: $i_n R_{th} = -3.88 V$ which equals v_{th} and is correct.